


Preparation branchement Leds ...

Materiels


1. 2 leds
2. 2 resistances
3. la soudure
4. la gaine thermo
5. 1 mini interrupteurs

schema Principe

1 Led

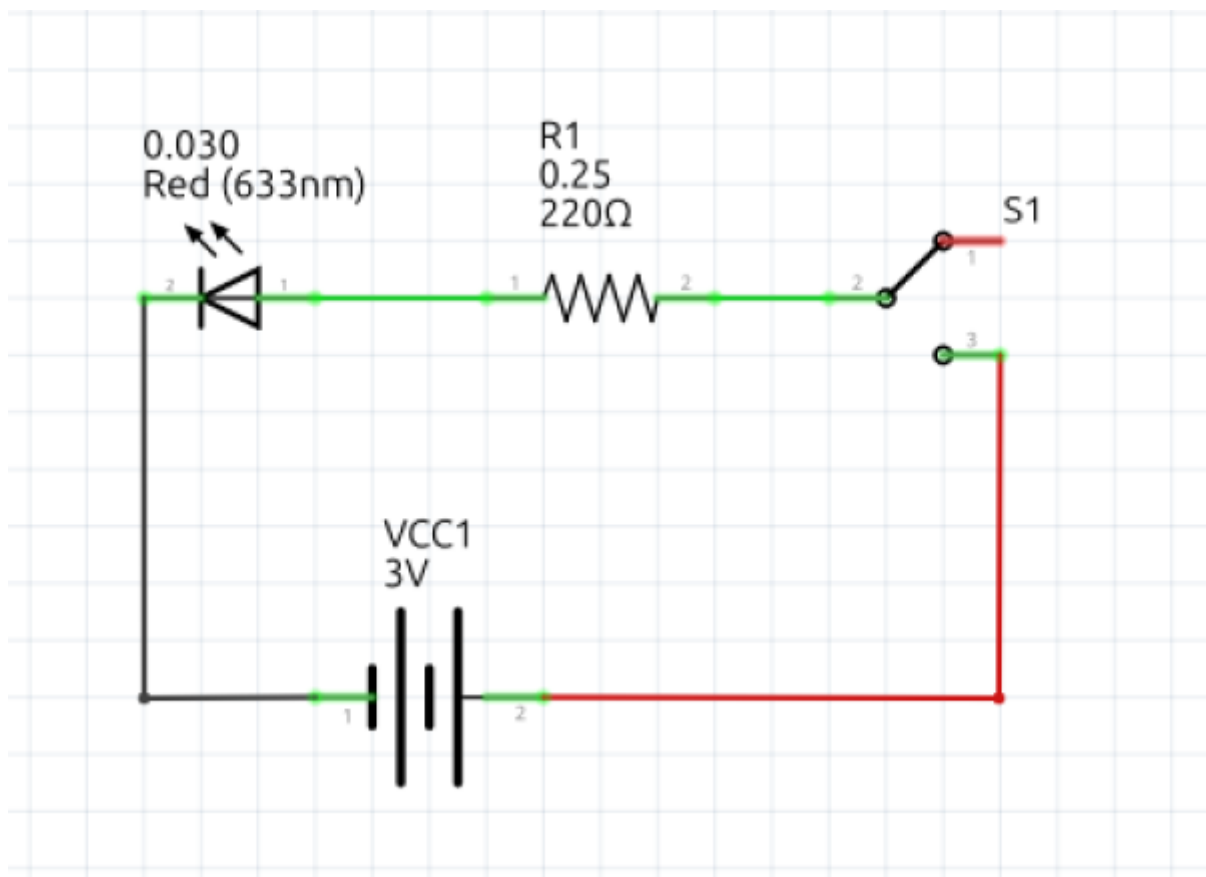


2 Leds

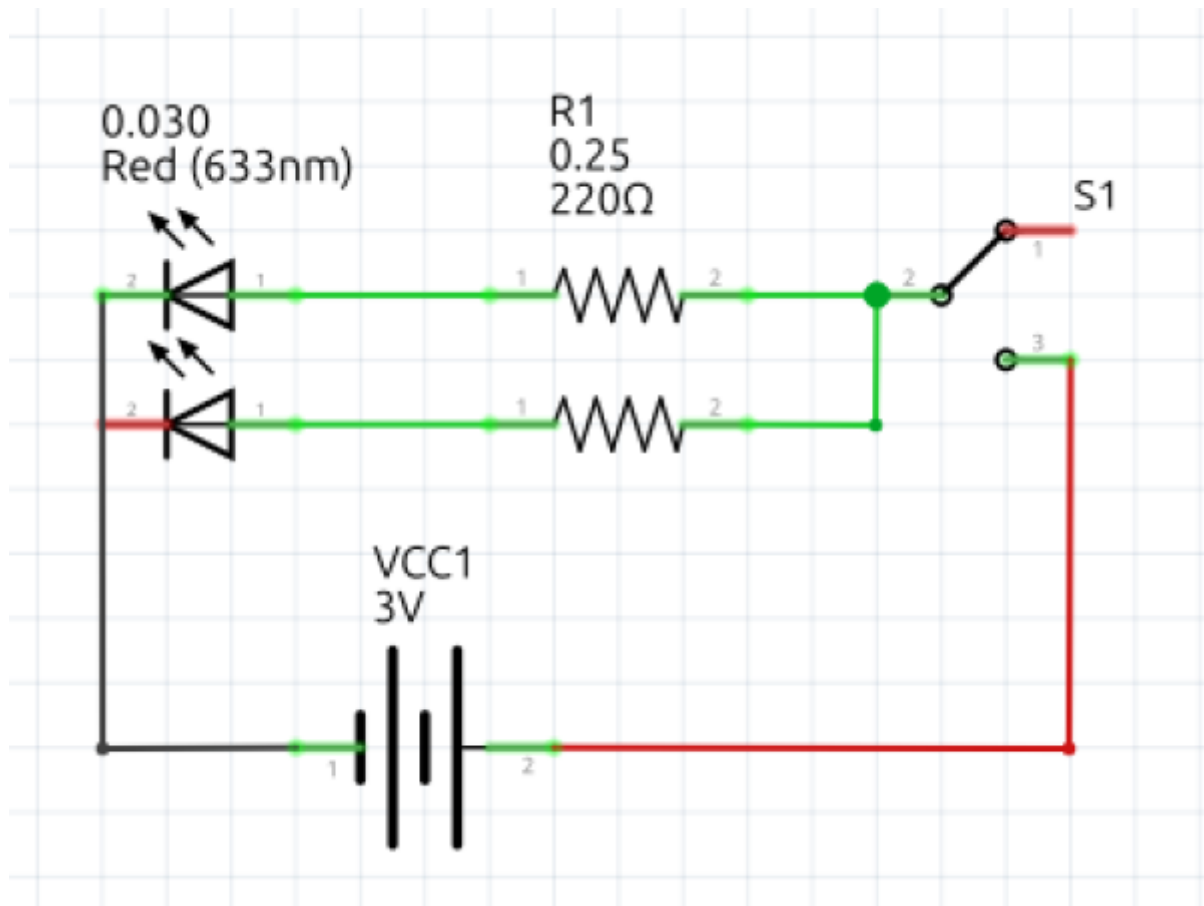


Schema cablage

1 led

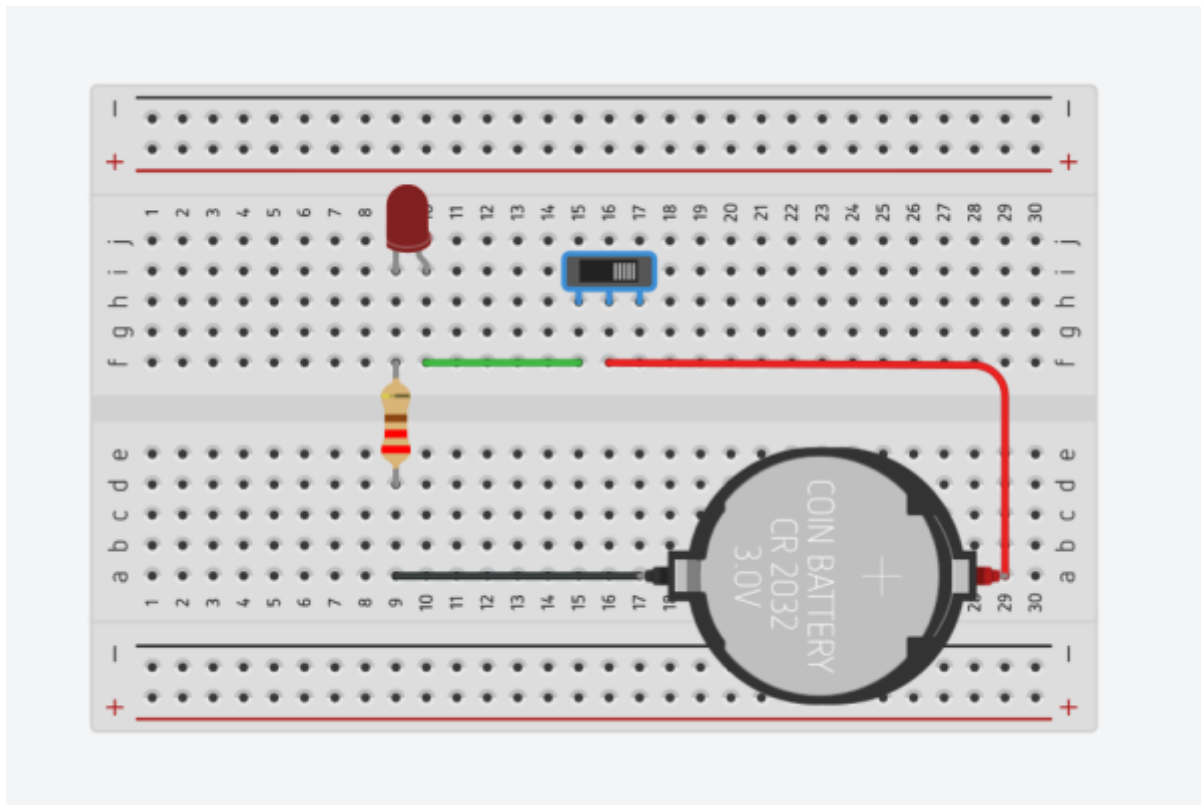


2 leds

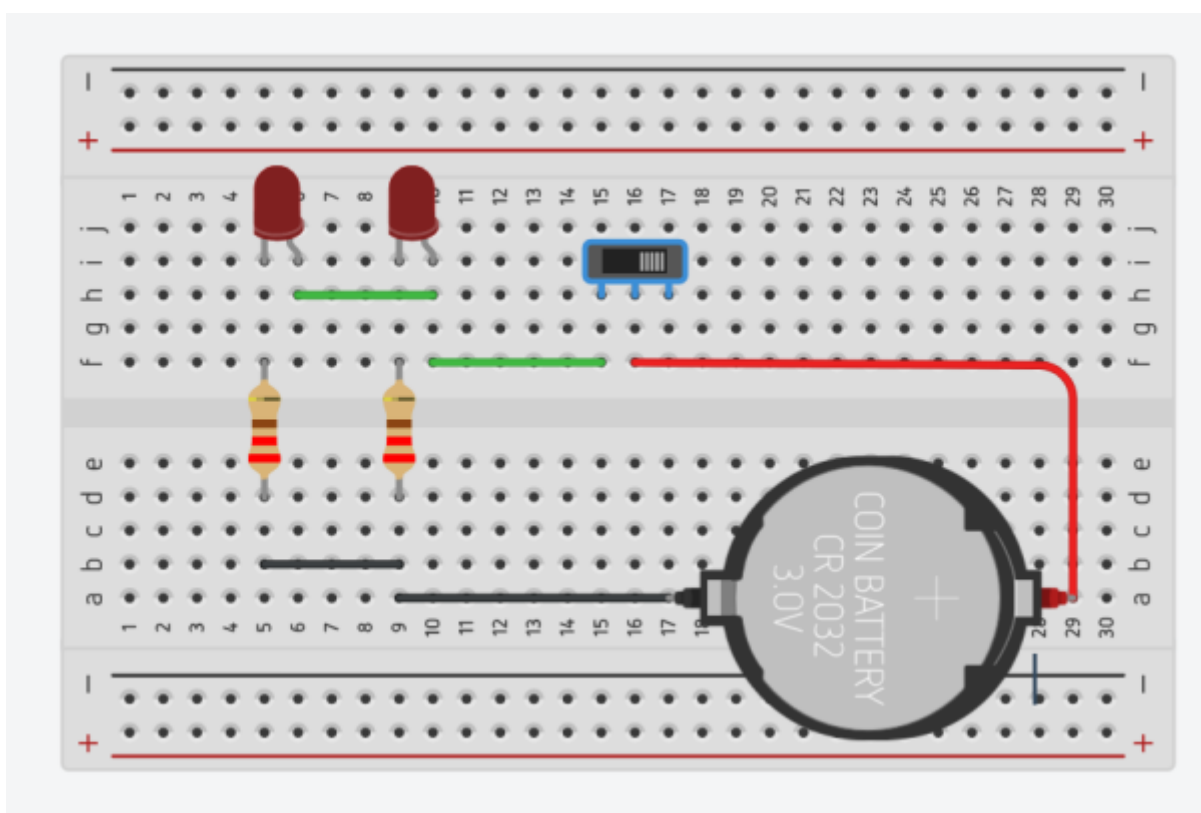


2 leds sur Tinkercad

Led Clignotante

schema principe

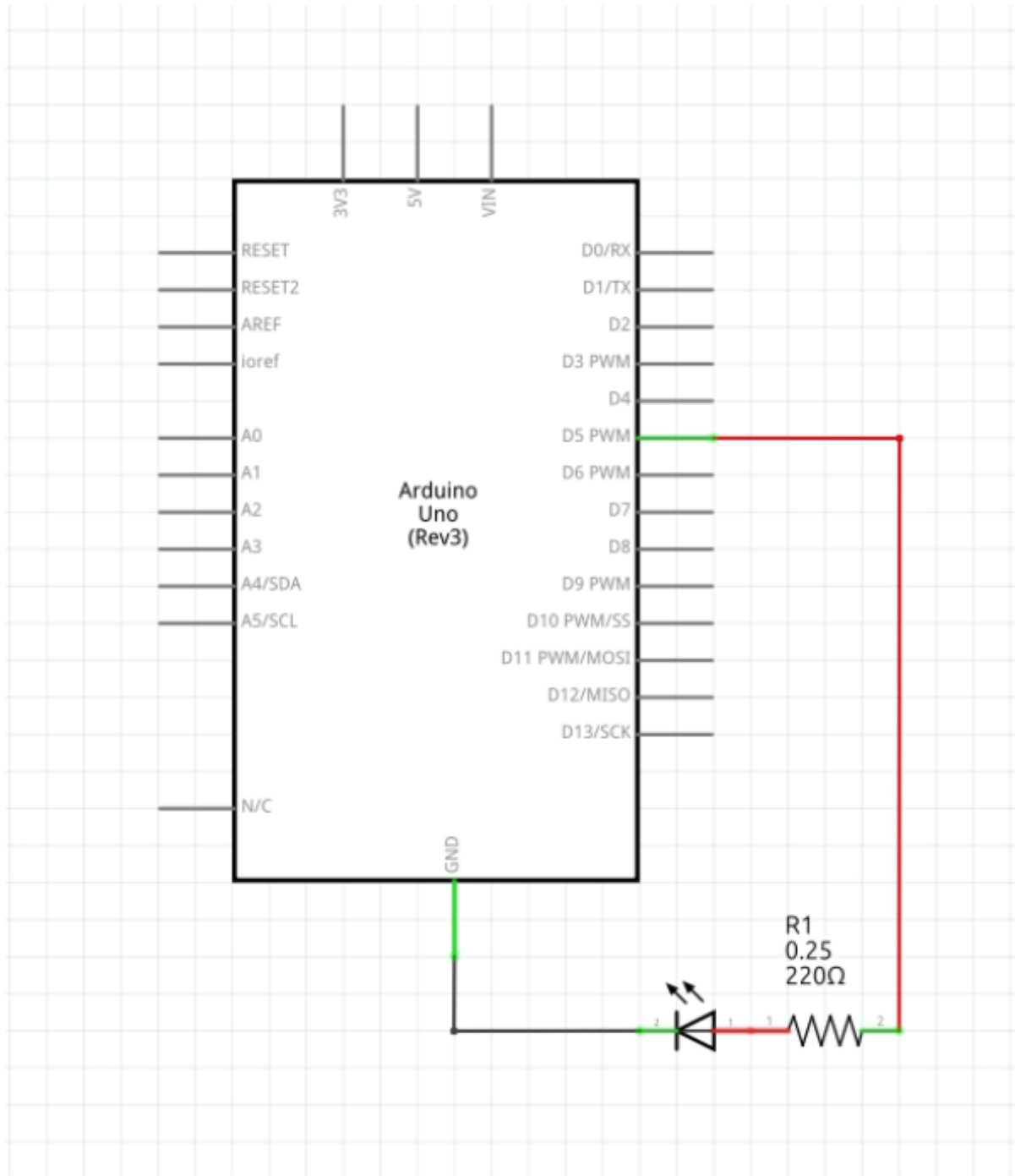

Schema cablage

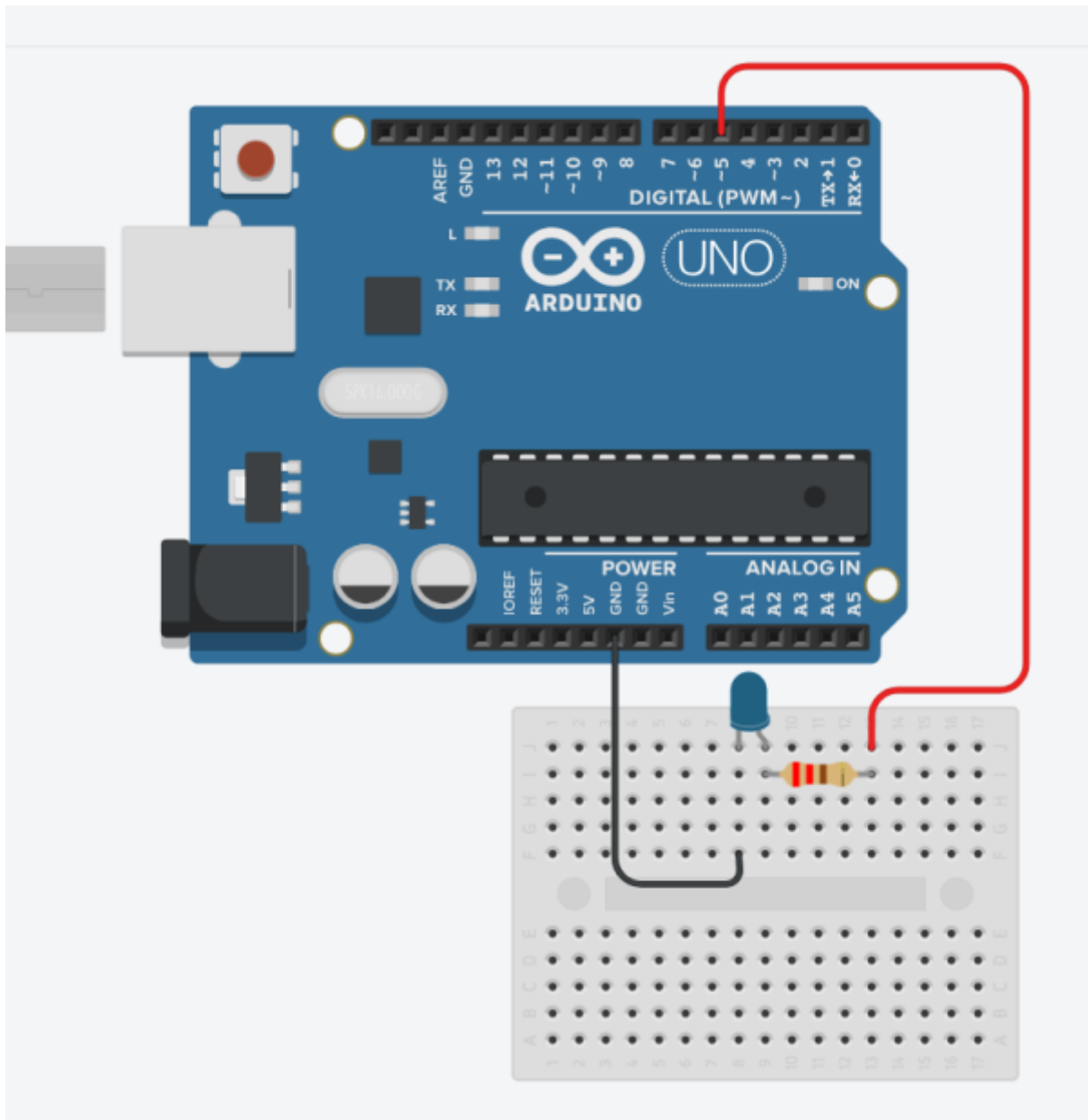

Code

mode texte

ledclignote.ino

```
// C++ code
//
void setup()
{
  pinMode(5, OUTPUT);
}

void loop()
{
  analogWrite(5, 1);
}
```

```
delay(1000); // Wait for 1000 millisecond(s)
analogWrite(5, 0);
delay(1000); // Wait for 1000 millisecond(s)
}
```

mode bloc



Last
update: start:jeunes:prepa:branceleds https://chanterie37.fr/fablab37110/doku.php?id=start:jeunes:prepa:branceleds&rev=1759346922
2025/10/01 21:28

From:
<https://chanterie37.fr/fablab37110/> - **Castel'Lab le Fablab MJC de Château-Renault**

Permanent link:
<https://chanterie37.fr/fablab37110/doku.php?id=start:jeunes:prepa:branceleds&rev=1759346922>

Last update: **2025/10/01 21:28**

